
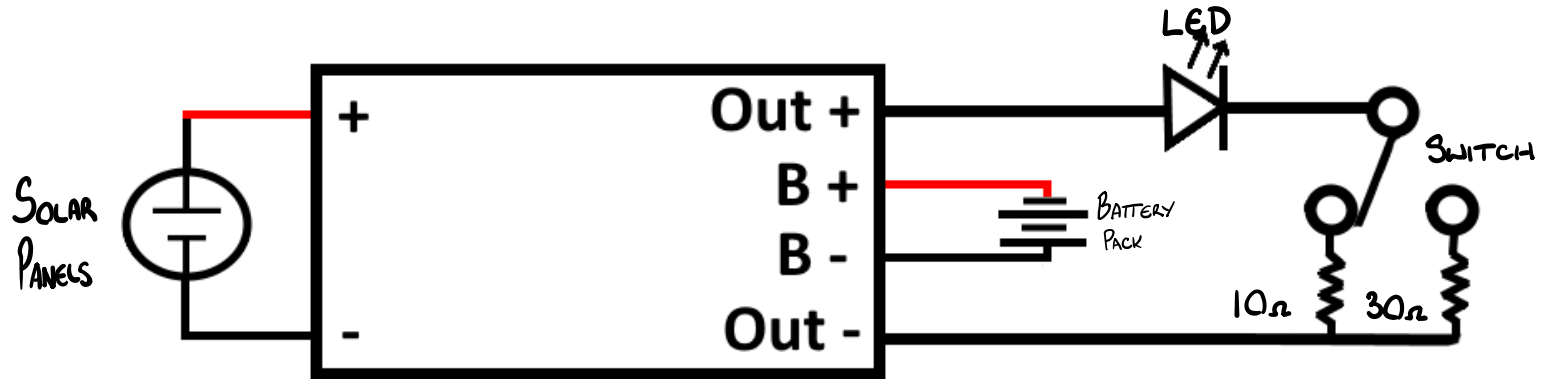



# CIRCUIT DIAGRAM

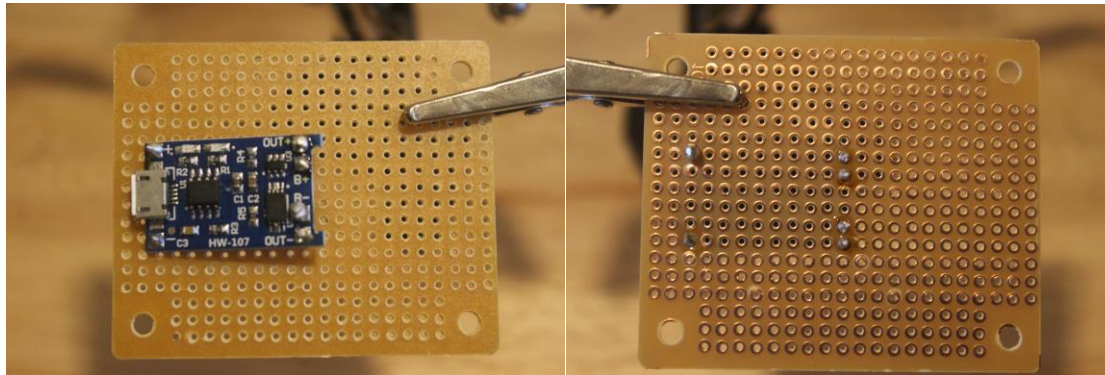


**Step 1:** Solder Battery Charger to perf board



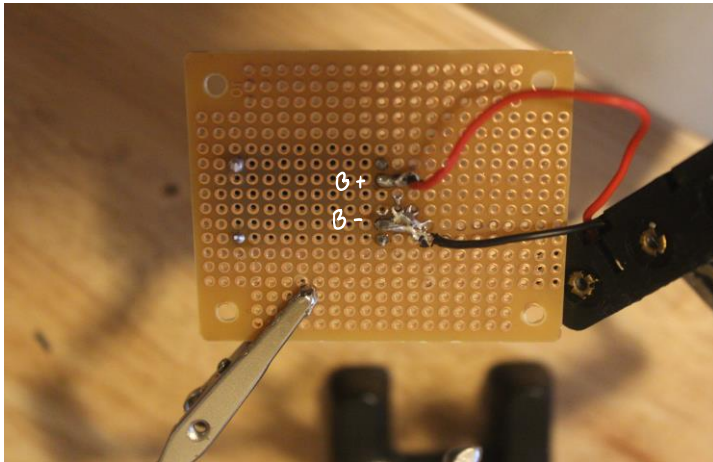**Step 2:** Solder Battery Pack to B+ and B- pins. ( RED to B+, BLACK to B- )




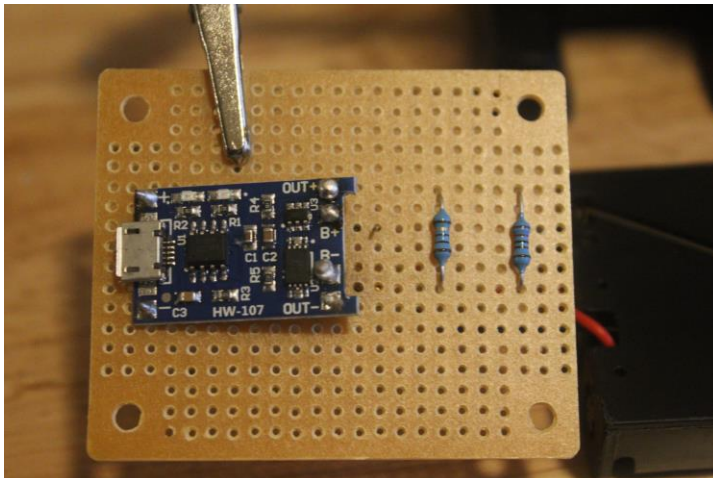**Step 3:** Solder 30 ohm and 10 ohm resistor to board



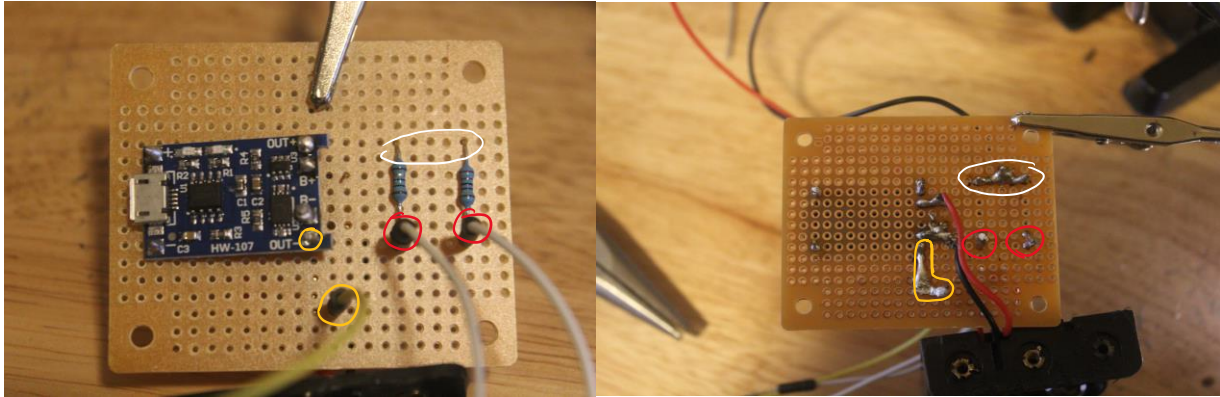**Step 4:** Add the wires for the 2-way switch. The nodes on the “top end” of both resistors should be soldered together, but the bottom nodes where the wires connect **MUST BE SEPARATE**. The third wire is then soldered to the OUT- node







**Step 5:** Solder the wires connecting to the resistors individually to the each outside prong of the switch, then solder the wire connected to the OUT- node to the middle prong of the switch.



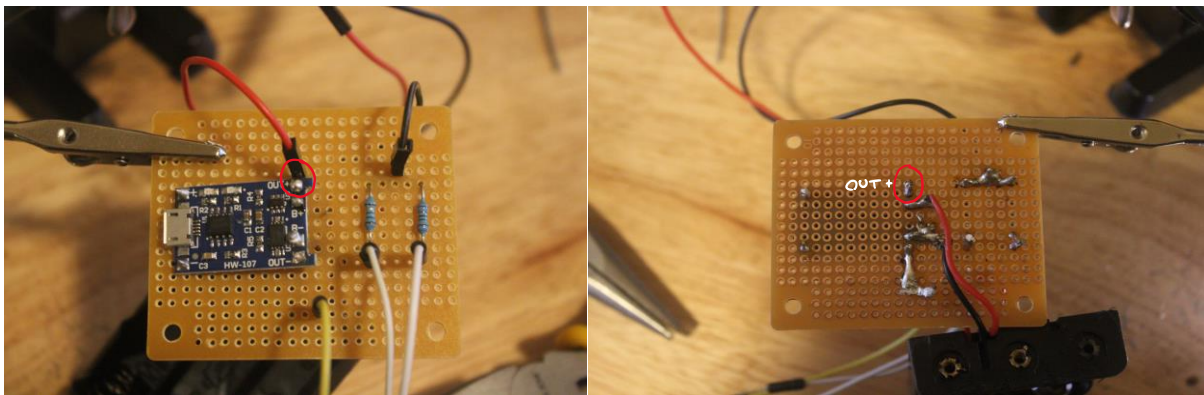**Step 6:** Adding the wires for the LED. Solder a male to female wire to the OUT+ node, and a male to female wire to the node connecting the top end of the two resistors. Solder the male ends of the wires to the perf board.



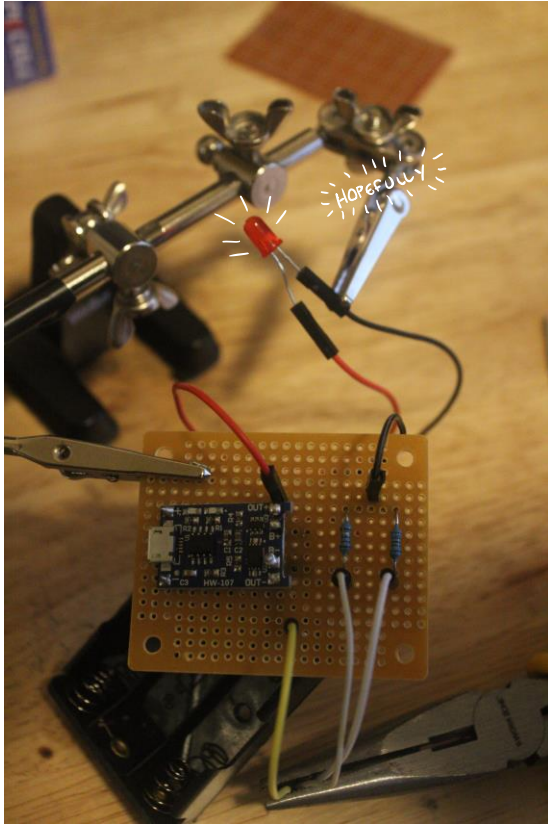**Step 7:** Add batteries and LED to check if the 2-way switch circuit is working properly.



**Step 8:** Solder solar panel wires to their corresponding + and – inputs of the perf board.

( RED is + Black is - )

ANT IS  
TAKING PIC  
TIGHT