



Sign In!

Audio EQ Workshop



Spring 2024





What you'll learn about

- Soldering
- RC Circuits
- Filters
- Audio
- Frequency Spectrum











What is an EQ?

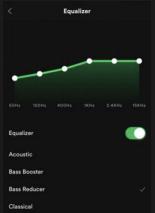
- Audio can be split in three basic frequency ranges: low, mid, high
- Can visualize audio using a Frequency spectrum
- If we want to increase/decrease sound level of frequencies, use an EQ




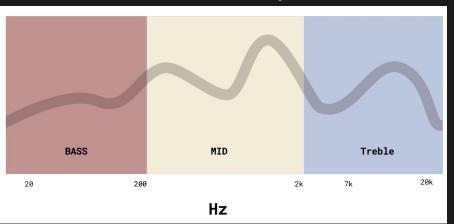



Other Examples

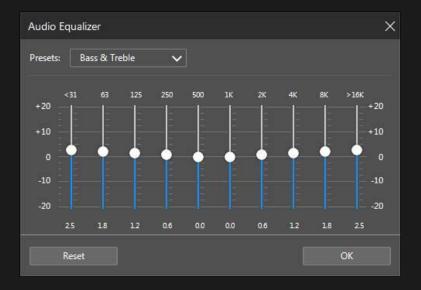

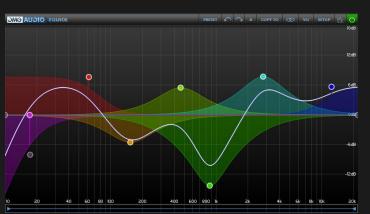









homieees in the studio like


How does it work?

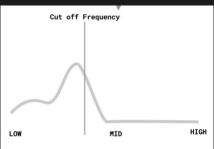

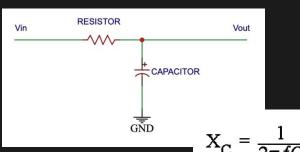





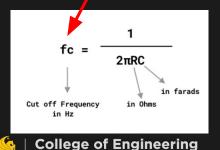- RC Passive Filters!
 - Made up of resistors and capacitors
- Capacitor reactance formula
 - As frequency increases, resistance decreases, voltage decreases
- Low Pass & High Pass Filter
 - Allows desired frequencies to pass
 - Cutoff Frequency determines where undesired frequencies roll off
 Potentiometers change resistance



and Computer Science

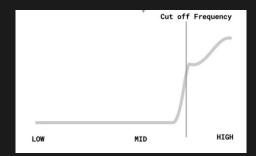


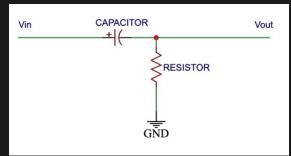




How does it work?


Band Pass = Low Pass + High Pass

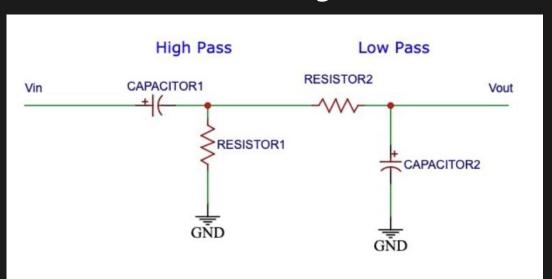

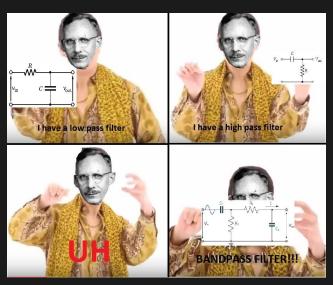





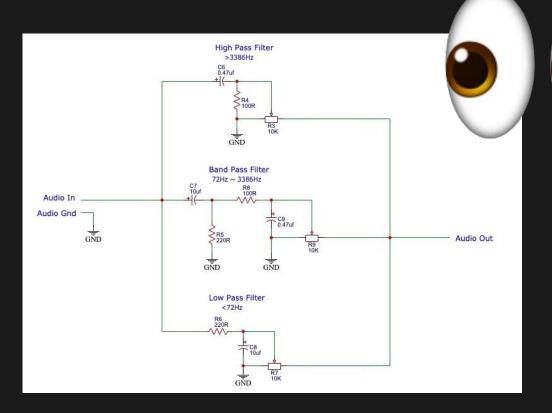






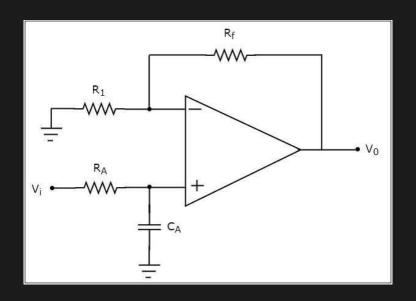Problem with Passive Filters

- When you attach something to the output, the voltage drops
 - This means lower volume
- Fix: Active filters
 - Amplification







How to Solder and not burn yourself lol










Wiring of the Solder Board

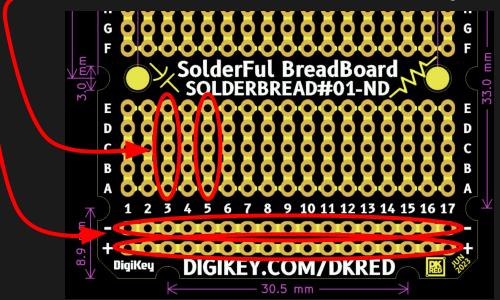- Positive and negative (ground) rails are wired horizontally
 - Other connections are wired vertically









Now Go~~~!

- Open up instructions in Google Docs
- Ask for help if you need!

https://docs.google.com/document/d/1ylOzbRfCS3_CaZcGtvx9tQ1rc6Y3ogl

mPakmMxCU1as/edit?usp=sharing







Interested in joining Workshop Committee?



MY MAN

Come talk to us!

Or message Ethan on Discord





